

2023

COMPUTER SCIENCE — GENERAL

Paper : GE/CC-1

(Computer Fundamentals and Digital Logic Design)

Full Marks : 50

The figures in the margin indicate full marks.

*Candidates are required to give their answers in their own words
as far as practicable.*

Answer **question no. 1** and **any four** questions from the rest.

1. Answer **any five** questions :

2×5

- (a) Define Data and Information.
- (b) Write names of any four system software.
- (c) What is line editor?
- (d) Explain the concept of parallel machines.
- (e) Convert $(ABC)_{16}$ and $(678)_8$ to binary.
- (f) What is a flip flop? Name two flip flops other than SR flip flop.
- (g) State De Morgan's Theorem for two variables.
- (h) Write the function of multiplexer.

2. (a) Write notes on Generations of Computers.

(b) State the differences between high level languages and low level languages.

(c) What is a pseudocode?

5+3+2

3. (a) Simplify the following Boolean function using Karnaugh Map and draw logic circuit of the simplified function :

$$F(A,B,C,D) = \sum (1,3,5,7,8,9,10,11)$$

(b) Explain with example the main symbols used for drawing a flowchart.

(3+2)+5

4. (a) Find the following :

(i) 2's complement of $(11010011)_2$

(ii) 9's complement of $(1234)_{10}$.

(b) What are the Error Detecting Codes? Give two examples.

(c) Write truth table of a full adder and draw its logic diagram.

(2+2)+3+3

Please Turn Over

5. (a) Define universal gate. Prove that NOR is a universal gate.
(b) State the differences between combinational and sequential circuits, giving example of each
(c) What is a comparator? (1+3)+4+2

6. (a) Given a SR flip-flop, perform the following :
(i) Draw its logic diagram.
(ii) Draw its truth table.
(iii) Draw its excitation table.
(iv) Write its characteristic equation.
(b) Why is cache memory used? (2+2+2+2)+2

7. (a) What is a decoder? Draw truth table and logic diagram of a 3-to-8 decoder.
(b) Draw logic circuit of a right shift register and explain its operation. (2+4)+4

8. Write short notes on *any two* of the following : 5×2

- (a) Computer virus and protection from virus
(b) Language Translators
(c) Alphanumeric Codes
(d) Asynchronous Counters.
-