

2023

## COMPUTER SCIENCE — MDC

Paper : CC-1

Full Marks : 75

*The figures in the margin indicate full marks.**Candidates are required to give their answers in their own words as far as practicable.*Answer **question no. 1** and **any three** questions from **Section - A** and **any five** questions from **Section - B**.1. Answer **any five** of the following :

2×5

- Write two differences between low-level and high-level languages.
- Find out the octal representation of  $(1F5 \cdot A2)_{16}$ .
- Prove that  $X + Y \cdot Z = (X + Y) \cdot (X + Z)$ , where X, Y and Z are Boolean variables.
- Design a two input AND gate using a  $2 \times 1$  multiplexer.
- What is a common anode type seven segment display?
- State the advantages of using synchronous counters over asynchronous counters.
- Mention the differences between sequential and combinational circuits.
- What is Delay flip-flop?

## Section - A

- Explain the working of a 4-bit binary adder-subtractor circuit with a neat diagram. 5
- What is a magnitude comparator? Design a 1-bit comparator using NAND gates. 2+3
- Convert a D flip-flop into a JK flip-flop. 5
- What do you mean by manchester code?
  - What are the differences between weighted and non-weighted code?
  - Convert  $(9CB)_{16} = ( )_2 ? = ( )_8?$  1+2+2
- Design a D flip-flop. 3+2
  - Convert it to Toggle flip-flop.

## Section - B

7. (a) Define half adder.  
 (b) Implement a full adder using two half adders.  
 (c) Why do we call decoders as min-term generators? Explain with an example. 2+3+5
8. (a) State De-Morgan's theorems.  
 (b) Convert into canonical POS.  $Y = AB + BC$ .  
 (c) Simplify the expression given below and draw the diagram by NAND gates :  
 $Y = \Sigma_m(1, 2, 6, 7, 8, 13, 14, 15) + \Sigma_d(0, 3, 5, 12)$ . 2+3+5
9. (a) Define full subtractor.  
 (b) Implement a full subtractor using a  $4 \times 1$  multiplexer.  
 (c) Why demultiplexers are called data distributors?  
 (d) Design an even parity checker. 2+3+3+2
10. (a) Subtract  $24_{10}$  from  $14_{10}$  by 2's Complement method.  
 (b) Fill in the blank :  $(17)_{10} + (21)_8 - (0F)_{16} = ( ? )_2$ .  
 (c) State the differences among Super, Mainframe, Mini and Personal Computer. 3+3+4
11. (a) Define propagation delay and noise margin in a logic gate.  
 (b) Convert  $(10110111)_2$  into gray code.  
 (c) Design a Johnson Counter using D flip-flops. 4+2+
12. Design 32 to 1 multiplexer using 8 to 1 multiplexers. — Explain with truth table. 1
13. (a) Design a priority encoder using basic logic gates and give the truth table.  
 (b) Realize a 2 to 4 decoder using NAND logic gates. 5+
14. (a) What is the truth table of a JK latch? From that deduce the characteristic equation, hence draw JK latch using NAND gates.  
 (b) Define the race around condition of JK flip-flop and hence explain how master-slave JK flip-flop overcomes this issue. 5