

2023

COMPUTER SCIENCE — HONOURS

Paper : CC-1

(Digital Logic)

Full Marks : 50

*The figures in the margin indicate full marks.**Candidates are required to give their answers in their own words as far as practicable.*Answer **question no. 1** and **any four** questions from the rest.

1. Answer **any five** questions : 2×5
- Construct a XOR gate (2 input) using minimum number of two input NAND gates.
 - What is principle of duality?
 - What is S-R flip flop?
 - What is SOP? Give suitable example.
 - Convert the BCD number 0111 1100 0011 to its decimal equivalent.
 - What is negative edge triggered clock pulse?
 - Simplify the boolean expression $x = A \cdot B \cdot C + A \cdot \bar{B} (\overline{A \cdot C})$ and implement it using fundamental/basic logic gates.
 - Design OR gate using 2-input NAND gates.
2. (a) What is a 3-bit full adder? Draw the truth table of a full adder. Derive the boolean expression for sum output and carry output from the truth table. Draw the logical circuit diagram using basic logic gates.
- (b) Show that XOR gate can be used as control inverter. Give appropriate examples. (2+2+2+2)+2
3. (a) Draw the logic circuit diagram of master slave J-K flip flop using NAND gates and explain its operation and also draw the truth table.
- (b) State and prove De-Morgan's theorem with appropriate example. 7+3
4. (a) Simplify the logic expression $F = \sum_m (1,4,6,8,9)$ using K-map. Draw the truth table and implement the simplified expression using basic logic gates.
- (b) What is race-around problem? Give examples. 7+3

Please Turn Over

5. (a) Design a 3-bit full subtractor using two 4×1 multiplexers and other logic gates. Draw the truth table. 6+4
(b) Draw the logical circuit diagram of a de-bouncer circuit using two input NAND gates.
6. (a) Implement a half adder using 4 to 1 multiplexer and other necessary logic gates. Explain the design and draw the appropriate logic circuit diagram. 6+4
(b) Realize XOR logic using NAND logic gates.
7. (a) Construct a decade up 4-bit ripple asynchronous counter using J-K flip flop and explain its operation with appropriate illustration. 8
(b) What is even parity generator? 5
8. Write short notes on (*any two*) :
- (a) TTL two input NAND gate
 - (b) Universal shift register
 - (c) Johnson Counter
 - (d) Seven Segment display.
-